



B.E. DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018)

Second Semester

ELECTRONICS AND INSTRUMENTATION ENGINEERING

U18EII2201: Foundation in Electrical and Electronics Engineering

COURSE OUTCOMES

- CO1:** Analyze the given DC circuits and AC resonant circuits.
CO2: Solve the given networks by applying circuit theorems.
CO3: Explain the characteristics and applications of various electronic devices.
CO4: Illustrate the concepts of Electrical Machines and Transformers.
CO5: Simulate and analyze the given Electrical and Electronics circuit.

Time: Three Hours


Maximum Marks: 100

Answer all the Questions
PART A (10 x 2 = 20 Marks)
(Answer not more than 40 words)


- | | |
|--|-----------------------|
| 1. Define charge. | CO1 [K ₁] |
| 2. State Kirchhoff's Laws. | CO1 [K ₁] |
| 3. State Norton's Theorem. | CO2 [K ₁] |
| 4. What is the limitation of maximum power transfer theorem? | CO2 [K ₁] |
| 5. Define intrinsic standoff ratio of UJT. | CO2 [K ₁] |
| 6. Why MOSFET is called voltage controlled device? | CO3 [K ₂] |
| 7. Define Latching Current. | CO3 [K ₁] |
| 8. List the applications of LED. | CO3 [K ₁] |
| 9. Why transformer rating is in kVA? | CO4 [K ₂] |
| 10. Why single phase induction motors are not self starting? | CO4 [K ₂] |

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

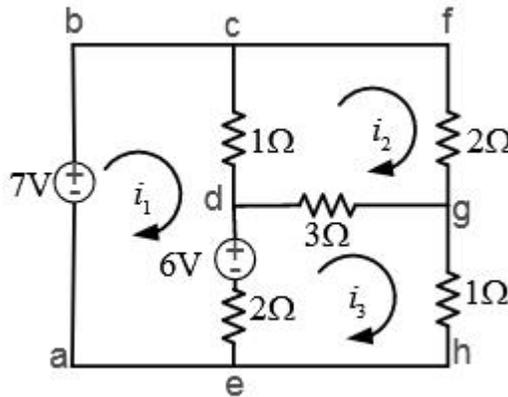
11. a) Compare series and parallel circuits with suitable examples. 6 CO1 [K₂]
 b) Determine the current i_1 , i_2 and i_3 of the given network by mesh current method. 10 CO1 [K₃]



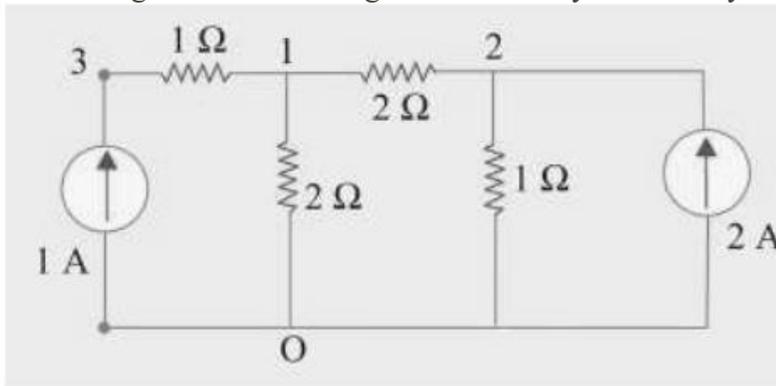12. Determine the voltages 1 and 2 of the given network by nodal analysis method. 16 CO1 [K₃]



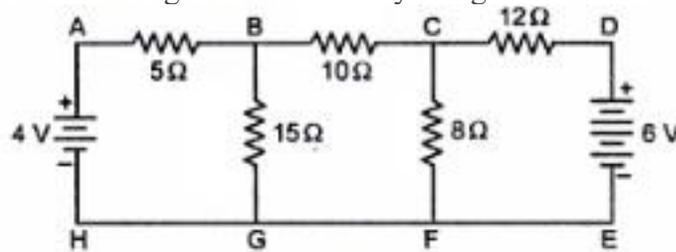13. Calculate the current through 10 Ω resistor by using Thevenin's theorem. 16 CO2 [K₃]



14. a) Explain the V-I characteristics of p-n Junction diode. 8 CO3 [K₂]
 b) Discuss the working principle of NPN type transistor operated under CE configuration. 8 CO3 [K₂]
15. Explain the V-I characteristics of SCR with neat diagrams 16 CO3 [K₂]
16. a) With a neat sketch, describe the constructional features and working principle of DC Motors. 8 CO4 [K₂]
 b) With a neat sketch, describe the constructional features and working principle of three phase Induction Motors. 8 CO4 [K₂]
