



B.TECH. DEGREE EXAMINATIONS: APRIL / MAY 2023

(Regulation 2018)

Second Semester

INFORMATION TECHNOLOGY

U18ITI2201: Digital Logic and Microprocessor

COURSE OUTCOMES

CO1: Demonstrate the knowledge of logic gates, Boolean algebra, minimization techniques and apply to design a combinational circuit.

CO2: Analyse and design sequential circuits.

CO3: Program 8086 for the given problems.

CO4: Interface 8086 with peripheral devices.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions: -


PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

- | | | |
|--|-----|-------------------|
| 1. What are the different kinds of methods adapted to reduce Boolean function. | CO1 | [K ₁] |
| 2. Define duality property. | CO1 | [K ₁] |
| 3. Draw the block diagram of a sequential circuit. | CO1 | [K ₂] |
| 4. Illustrate the circuit diagram to convert a T-FF into a D-FF. | CO2 | [K ₂] |
| 5. Define state diagram. | CO2 | [K _L] |
| 6. What is meant by programmable counter? | CO2 | [K ₁] |
| 7. Define the term ALE in 8086. | CO3 | [K ₁] |
| 8. List the general-purpose registers in 8086. | CO3 | [K ₁] |
| 9. Recall the master-slave connection in 8259. | CO4 | [K ₁] |
| 10. Classify data transfer types supported by 8237? | CO4 | [K ₂] |

**Answer any FIVE Questions: -
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)**

- | | | | | |
|-----|---|----|-----|-------------------|
| 11. | a) Determine the combination circuit for Half adder. | 4 | CO1 | [K ₂] |
| | b) Using a Karnaugh map method obtain the minimal SOP and POS expressions for the given function. $F(x, y, z, w) = \sum m(1, 3, 4, 5, 6, 7, 9, 12, 13)$ | 12 | CO1 | [K ₂] |
| 12. | Minimize the following using Karnaugh map. Implement the relevant function using NOR gates only, $F(A, B, C, D, E) = \pi M(2, 4, 7, 9, 26, 28, 29, 31)$ | 16 | CO1 | [K ₃] |
| 13. | a) Explain the working principle of master-slave JK flip-flop. | 8 | CO2 | [K ₂] |
| | b) Outline the circuit of clocked RS flip-flop and explain with truth table. | 8 | CO2 | [K ₂] |
| 14. | a) Distinguish between the Moore machine from Mealy machine. | 4 | CO2 | [K ₄] |
| | b) For the state diagram shown in given figure, design a synchronous sequential circuit using JK flip-flop. | 12 | CO2 | [K ₂] |

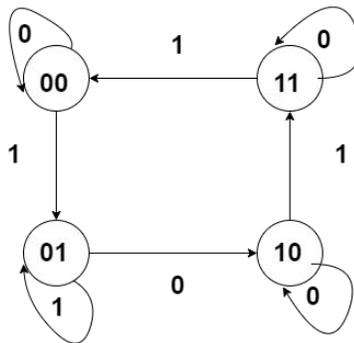

- | | | | | |
|-----|--|----|-----|-------------------|
| 15. | a) Explain the addressing modes of 8086 with examples. | 10 | CO3 | [K ₂] |
| | b) Interpret the following assembly directives.
i) SHORT; ii) TYPE; and iii) FAR PTR | 6 | CO3 | [K ₂] |
| 16. | a) Illustrate and explain the interfacing between 8086 and two 8259 PIC connected in master-slave configuration. | 8 | CO4 | [K ₂] |
| | b) Briefly explain the functions of 8255. | 8 | CO4 | [K ₂] |
