



**B.E/B.TECH DEGREE EXAMINATIONS: APRIL /MAY 2024**

(Regulation 2018)

Fourth Semester

**ELECTRONICS AND COMMUNICATION ENGINEERING**

U18ECI4202: Analog Electronics and Integrated Circuits

**COURSE OUTCOMES**

- CO1: Design and verify feedback amplifiers, LC and RC oscillators.  
 CO2: Describe the characteristics of operational amplifiers.  
 CO3: Develop and analyze operational amplifier application circuits.  
 CO4: Build data converters for the given specifications.  
 CO5: Operate 555 timer circuit and generate waveforms.

**Time: Three Hours**

**Maximum Marks: 100**

**Answer all the Questions:-**

**PART A (10 x 2 = 20 Marks)**

**(Answer not more than 40 words)**

- |  |     |                   |
|--|-----|-------------------|
| 1. Compare and contrast positive and negative feedback in amplifier.   | CO1 | [K <sub>2</sub> ] |
| 2. What are the conditions for sustained oscillation in an oscillator?   | CO1 | [K <sub>2</sub> ] |
| 3. List the importance of current mirror circuit used in differential amplifier.   | CO2 | [K <sub>3</sub> ] |
| 4. Draw the internal block diagram of an Op-amp  | CO2 | [K <sub>3</sub> ] |
| 5. Illustrate the need for an instrumentation amplifier.   | CO3 | [K <sub>2</sub> ] |
| 6. Summarize the applications of comparator.   | CO3 | [K <sub>2</sub> ] |
| 7. Why VCO is also called as V to F converter?   | CO5 | [K <sub>2</sub> ] |
| 8. An Astable multivibrator constructed using with 555 timer with $R_A=6.8k\Omega$ , $R_B=3.3k\Omega$ and $C=0.1\mu F$ . Compute $t_{HIGH}$ and $t_{LOW}$ .          | CO5 | [K <sub>3</sub> ] |
| 9. Evaluate the number of resistors required for an 8-bit weighted resistor D/A converter. Let the smallest resistance is R and obtain the largest resistance value. | CO4 | [K <sub>4</sub> ] |
| 10. Predict the number of comparators required for realizing a 4-bit flash ADC.  | CO4 | [K <sub>4</sub> ] |


**Answer any FIVE Questions:-**

**PART B (5 x 16 = 80 Marks)**

**(Answer not more than 400 words)**

- |  |   |     |                   |
|--|---|-----|-------------------|
| 11. a) Explain the working of an RC phase shift oscillator with neat circuit diagram and derive an expression for frequency of sustained oscillations. | 8 | CO1 | [K <sub>2</sub> ] |
|--|---|-----|-------------------|

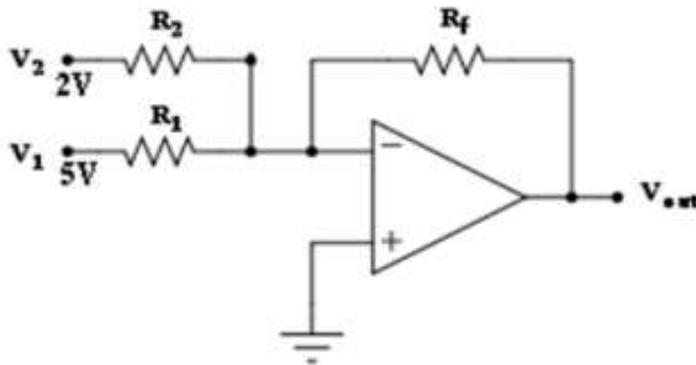- b) Draw the current series feedback amplifier and derive the equation for the input impedance, output impedance and the voltage gain. 8 CO1 [K<sub>2</sub>]
12. a) Construct the tank circuit of Hartley oscillator for the frequency of 120KHz, L<sub>1</sub>=0.4mH and C=0.004μF. Neglect the mutual inductance. 6 CO2 [K<sub>3</sub>]
- b) Illustrate the DC characteristics of operational amplifier. Also explain the compensation techniques used. 10 CO2 [K<sub>2</sub>]
13. a) Describe the working of an integrator using Op-amp. Also draw the input and output waveform of practical integrator when the input is sine wave and square wave. 12 CO3 [K<sub>2</sub>]
- b) Examine the output voltage of the following circuit. Given R<sub>1</sub> =R<sub>2</sub> = 10kΩ and R<sub>f</sub> = 100 4 CO3 [K<sub>4</sub>]



- 14 a) Explain Log and Antilog log amplifier circuit with necessary diagrams. 8 CO3 [K<sub>2</sub>]
- b) Describe Schmitt Trigger circuit for V<sub>UT</sub>=3V and V<sub>LT</sub>= -IV. 8 CO3 [K<sub>4</sub>]
15. a) Discuss any two applications of PLL in detail. 6 CO5 [K<sub>2</sub>]
- b) Explain the working of 555 timer as Monostable Multivibrator. 10 CO5 [K<sub>2</sub>]
16. a) Examine the output voltage would be produced by a D/A converter for the output voltage range is 0 to 10V and its input binary number is,  
 i. 10(for a 2-bit D/A converter)  
 ii. 0110 (for a 4-bit D/A converter)  
 iii. 10111100(for a 8-bit D/A converter) 8 CO4 [K<sub>3</sub>]
- b) Explain the working of successive approximation type A/D converter. 8 CO4 [K<sub>2</sub>]

\*\*\*\*\*