



B.E/B.TECH DEGREE EXAMINATIONS: APRIL /MAY 2024

(Regulation 2018)

Fourth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING

U18EET4004: Network and System

COURSE OUTCOMES

- CO1: Understand the basic concepts of graph theory and apply it to electrical networks.
 CO2: Analyze the transient behavior of DC and AC circuits.
 CO3: Model the networks in S-domain and determine their equivalent two port network parameters.
 CO4: Design various types of filters, attenuators and observe their frequency response.
 CO5: Categorize the different types of signals and systems.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

1. Identify the number of branches in a Tree & Co-Tree for a graph which containing 5 nodes and 8 branches. CO1 [K₂]
2. List the properties of a tree. CO1 [K₁]
3. Determine the time constant of R-L series circuit shown in Figure 1. CO2 [K₂]

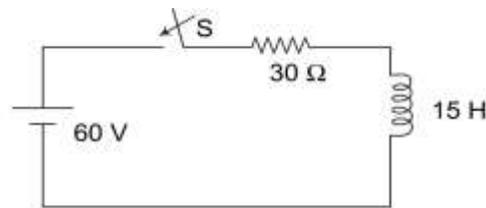


Figure 1

4. Draw the current response of a series R-C circuit when the circuit is excited by a DC source. CO2 [K₂]
5. Define a two-port network. CO3 [K₁]
6. What is meant by Poles and Zeros of a Network Function? CO3 [K₁]
7. Define band pass filter. CO4 [K₂]
8. Solve the one Decibel into Neper. CO4 [K₂]
9. List the various types of discrete time signals. CO5 [K₂]
10. Identify when a system is said to be casual and stable. CO5 [K₂]

**Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)**

11. a) If the tree of the graph shown in Figure 2 has branches 4, 5 and 6, then determine the tie-set matrix. 10 CO1 [K₃]

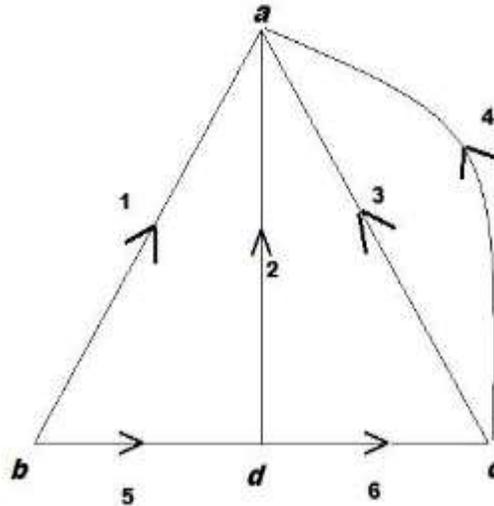


Figure 2

- b) Mention the properties of Incidence Matrix. 6 CO1 [K₁]
12. a) For the network shown in Figure 3, the switch K is closed at $t=0$ with zero initial current in the inductor. Find the values of I , di/dt , d^2i/dt^2 at $t=0$, if $R= 8\Omega$ and $L= 0.2 H$. 8 CO2 [K₃]

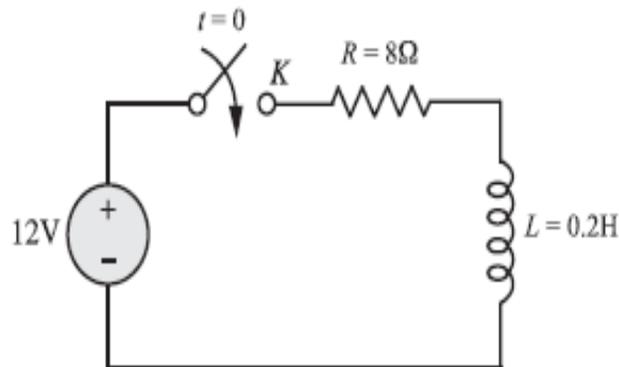


Figure 3

- b) Derive the current equation of a series R-L circuit driven by constant DC voltage source. Draw the current response curve. 8 CO2 [K₂]
13. a) Determine the incidence matrix of the graph in Figure 4. Also determine the 8 CO1 [K₃]

possible number of trees for this graph.

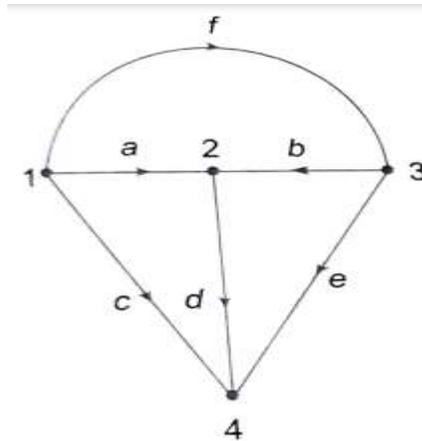


Figure 4

- b) Construct the Fundamental Cut-Sets of the circuit shown in Figure 5 considering the twigs as branches with 4 ohm resistors. 8 CO1 [K₃]

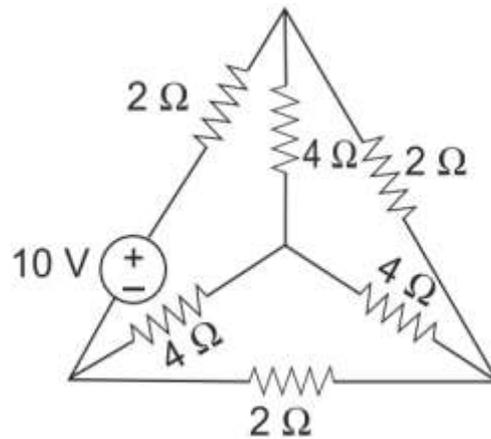


Figure 5

14. a) Determine the open circuit impedance (Z) parameters of the network shown in Figure 6. 8 CO3 [K₃]

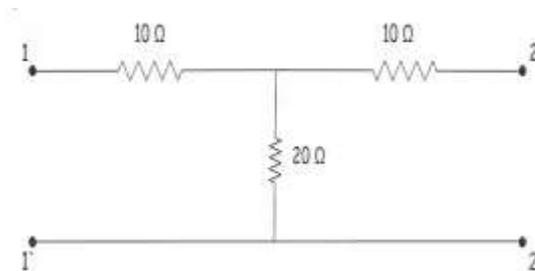


Figure 6

- b) Identify the Transform Impedance & Admittance of the network shown in Figure 7. 8 CO3 [K₃]

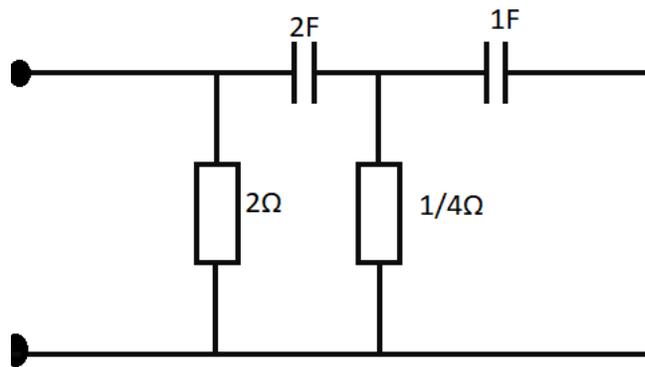


Figure 7

- | | | | | | |
|-----|----|--|----|-----|-------------------|
| 15. | a) | Derive the equation for characteristic impedance of a <i>T</i> filter network. | 8 | CO4 | [K ₂] |
| | b) | Develop the parameters of <i>T</i> -type Attenuator network. | 8 | CO4 | [K ₂] |
| 16. | a) | Determine whether the given system is casual or non-casual.
$y(n) = x(n) + 1/(x-1)$ | 12 | CO5 | [K ₃] |
| | b) | Illustrate the unit ramp function. | 4 | CO5 | [K ₂] |
