



B.E/B.TECH DEGREE EXAMINATIONS: APRIL/MAY 2024

(Regulation 2018)

Sixth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING

U18EEI6204: Solid State Drives

COURSE OUTCOMES

- CO1:** Compare various types of loads, quadrants of operation and characteristics of motors.
CO2: Design power converter circuits for DC and AC motor drives.
CO3: Describe the speed control schemes for DC and AC motor drives.
CO4: Choose the motor drives for appropriate applications.
CO5: Simulate AC and DC drive circuits using software tool.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

- | | | |
|---|-----|-------------------|
| 1. Identify the elements of electric drive system. | CO1 | [K ₁] |
| 2. Classify electrical braking of drives. | CO1 | [K ₂] |
| 3. A 200 V, 25 A, 1000 rpm separately excited DC motor is fed from single phase half-controlled converter and driving a constant torque load. Calculate the converter output voltage required to operate the motor at 500 rpm. Armature voltage drop is negligible. | CO4 | [K ₃] |
| 4. Construct three phase AC- DC converter circuit for 2 MW separately excited DC motor to operate in forward and reverse directions. | CO2 | [K ₃] |
| 5. Draw the circuit of DC- DC converter working in quadrants 1 and 3 to operate separately excited DC motor. | CO2 | [K ₃] |
| 6. A DC motor requires 60V input to the armature which is supplied from a DC-DC boost converter. Calculate the duty cycle of the boost converter with an input of 36 V from a battery. | CO5 | [K ₃] |
| 7. Draw the block diagram for constant V/f control of three phase induction motor. | CO3 | [K ₂] |
| 8. State the objective of vector control of three phase induction motor. | CO3 | [K ₃] |
| 9. Identify the applications of synchronous motor drives. | CO4 | [K ₂] |
| 10. List the simulation tools for electrical drives. | CO5 | [K ₂] |

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

11. a) (i) Describe acceleration, steady state operation and deceleration of electrical drives using torque balance equation. (4) CO1 [K₂]
(ii) Classify the loads with respect to speed- torque characteristics. (4)
- b) Illustrate the classes of motor duty with load curve and temperature curve. (8) CO1 [K₂]
12. a) Compare the circuits and operation of DC motor drives using single phase half-controlled converter and single phase fully controlled converter. (8) CO2 [K₂]
- b) Describe the circuit and waveforms of three phase fully controlled converter fed separately excited DC motor for continuous current mode. (8) CO2 [K₃]
13. a) With circuit diagram, explain the regenerative braking operation of DC motor using DC- DC boost converter. (6) CO3 [K₂]
- b) Describe the circuit and operation of four quadrant chopper fed separately excited DC motor. (10) CO2 [K₂]
14. a) Compare VSI fed induction motor drive and CSI fed induction motor drive. (6) CO2 [K₂]
- b) Describe the static method of rotor resistance control for three phase induction motor. If the external resistance is 8 Ω, internal rotor resistance is 3 Ω/ phase and duty cycle of control circuit is 0.5, calculate the effective value of resistance per phase in rotor circuit. (10) CO3 [K₃]
15. a) Illustrate a static method of slip power recovery for three phase slip ring induction motor. (8) CO2 [K₂]
- b) Describe the self- control method of synchronous motor drive using load commutated inverter. (8) CO3 [K₂]
16. a) Draw the block diagram of electric two-wheeler motor drive and explain the circuit for bipolar drive operation. (10) CO4 [K₂]
- b) Describe the process of paper mill and selection of drives. (6) CO4 [K₂]
