



B.E/B.TECH DEGREE EXAMINATIONS: APRIL /MAY 2024

(Regulation 2018)

Fourth Semester

ELECTRONICS AND INSTRUMENTATION ENGINEERING

U18EIT4005: Ancillary Support Systems

COURSE OUTCOMES

- CO1: Evaluate the basic principles of EMI/EMC problem identification, design, and prevention, Earthing and shielding principles, procedures and practices.
- CO2: Evaluate the principles of power distribution systems and system components.
- CO3: Develop a wiring diagram for a control panel.
- CO4: Illustrate the operation of hydraulic and pneumatic systems.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

- | | | |
|---|-----|-------------------|
| 1. Compare Relay and contactor. | CO3 | [K ₂] |
| 2. Short note on Fourier representation of EMI. | CO1 | [K ₂] |
| 3. Compare the function of circuit breaker and isolator | CO2 | [K ₄] |
| 4. Classify the insulation classes used in industries | CO2 | [K ₂] |
| 5. Summaries the safety and grounding technique used in electronics circuit. | CO1 | [K ₂] |
| 6. How do you calculate the internal resistance of a conductor? | CO2 | [K ₂] |
| 7. Why does most of the pressing machines operates with hydraulic system? | CO4 | [K ₄] |
| 8. State the selection procedure of variable frequency drive (VFD) | CO3 | [K ₂] |
| 9. What is the role of neutral and earth connection in the electrical circuit | CO2 | [K ₂] |
| 10. List the panel wiring accessories. | CO3 | [K ₂] |

Answer any FIVE Questions:-


PART B (5 x 16 = 80 Marks)

(Answer not more than 400 words)

- | | | | |
|--|----|-----|-------------------|
| 11. a) Explain the methodology used to detect EMI and analyze their performance and measures used to eliminates such problem | 10 | CO1 | [K ₄] |
| b) Analyze the power house safety and explain the protective methods | 06 | CO2 | [K ₂] |

- | | | | | | |
|-----|----|--|----|-----|-------------------|
| 12. | a) | Develop and explain a suitable electrical connection for the power distribution circuit using Three Source Single Bus with Bus Coupler with mechanical interlock | 10 | CO2 | [K ₃] |
| | b) | Describe the effect of stray capacitance fault occurring in the electronics circuits | 06 | CO1 | [K ₂] |

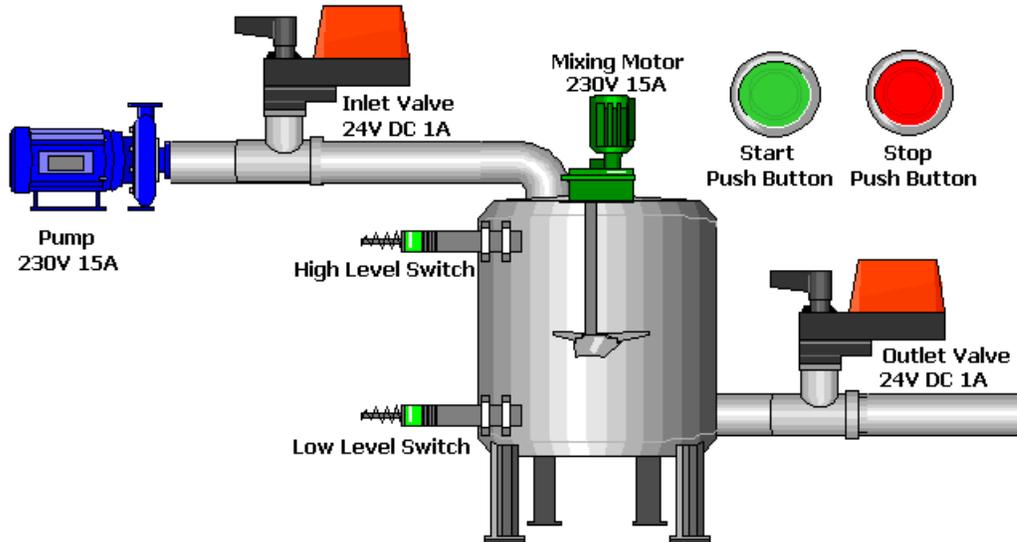Develop a Power and Control wiring for the following system



- | | | | | | |
|-----|--|--|----|-----|-------------------|
| 13. | | | 16 | CO3 | [K ₃] |
|-----|--|--|----|-----|-------------------|

Start PB and Low Level Switch – ON – Inlet Valve ON Then Pump ON
 When the High Level Switch – ON – Inlet Valve and Pump OFF Then Mixing Motor ON after delay 20 sec Mixing Motor OFF and Outlet Valve – ON
 When the Low Level Switch – ON – Outlet Valve - OFF

- | | | | | | |
|-----|----|--|----|-----|-------------------|
| 14. | a) | List and describe the types of direction control valves are involved in hydraulic and pneumatic circuits | 10 | CO4 | [K ₃] |
| | b) | Explain the operation of soft starter and list the merits and demerits | 06 | CO3 | [K ₂] |
| 15. | a) | Explain the different types of operation modes in variable frequency drive with suitable diagram | 10 | CO3 | [K ₂] |
| | b) | Build a suitable diagram and explain the hydraulic supply system | 06 | CO4 | [K ₂] |

Develop a electro-pneumatic circuit for the following condition

- | | | | | | |
|-----|--|---|----|-----|-------------------|
| 16. | | Start PB – ON Cylinder 1 Move Forward
When the cylinder 1 forward sensor – ON Cylinder 2 Move Forward
When the cylinder 2 forward sensor – ON then delay 10Sec
Both Cylinder move Reverse | 16 | CO4 | [K ₃] |
|-----|--|---|----|-----|-------------------|
