



B.E/B.TECH DEGREE EXAMINATIONS: NOV/DEC 2023

(Regulation 2018)

Third Semester

FASHION TECHNOLOGY

U18EEI3206: Basic Electrical and Electronics Engineering

COURSE OUTCOMES

- CO1:** Acquire basic knowledge on DC and AC circuits.
CO2: Understand the construction, working principle and applications of DC machines
CO3: Understand the construction, working principle and applications of AC machines and transformers.
CO4: Acquire basic knowledge on logic gates, semiconductor devices and their applications.
CO5: Identify electronic components and use them to design simple circuits.

Time: Three Hours


Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)

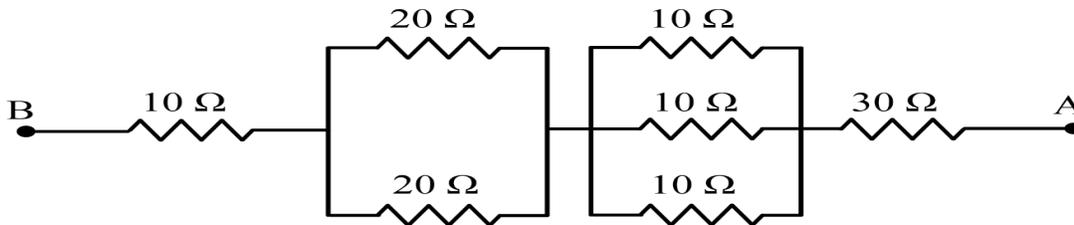
1. State Ohm's Law and mention its disadvantage CO1 [K₂]
2. What is the equivalent resistance between B and A? CO1 [K₃]




3. Draw the waveform and phasor diagram of pure inductive load connected in AC supply. CO2 [K₂]
4. Draw the Power triangle of AC circuit. CO2 [K₂]
5. Mention the function of commutator and brushes in DC generator. CO3 [K₂]
6. Why is the single-phase induction motor not self-starting? CO3 [K₂]
7. Mention the application of BJT in aircraft system. CO5 [K₃]
8. What are types of MOSFET? CO4 [K₂]
9. What are universal gates? Give example. CO5 [K₁]
10. Mention the function of decoder CO4 [K₂]

Answer any FIVE Questions:-
PART B (5 x 16 = 80 Marks)
(Answer not more than 400 words)

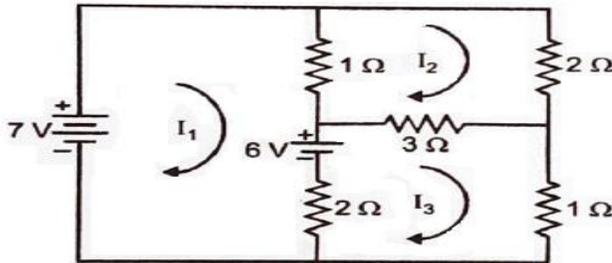11. a) Explain the Kirchhoff's voltage and current laws with example. 6 CO1 [K₂]
 b) Use mesh analysis to determine the three mesh currents in the circuit of figure shown in below. 10 CO1 [K₂]



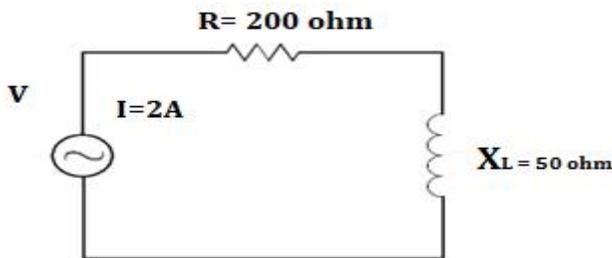12. a) Explain the behavior of AC in RL series circuit with waveform and Phasor diagram. 10 CO2 [K₃]
 b) A 200 Ω resistor and a 50 Ω X_L are placed in series with a voltage source, and the total current flow is 2 amps, as shown in Figure. 6 CO2 [K₃]



Find the Power Factor(pf),Applied voltage V, Real Power P.

13. a) Describe the construction of DC machine with neat diagram. 10 CO3 [K₂]
 b) Explain the operation of single-phase capacitor start induction motor. 6 CO3 [K₂]
14. a) Explain the working of PN junction diode and draw its V-I characteristics. 8 CO4 [K₂]
 b) Discuss about the operation of Full wave rectifier with waveforms. 8 CO4 [K₂]
15. a) Explain the full adder circuits with truth table and logic diagram. 8 CO5 [K₂]
 b) Describe about working of 1 to 4 multiplexer with block diagram and truth table. 8 CO5 [K₂]
16. a) Draw and explain the input and output characteristics of CE configuration of transistor. 8 CO4 [K₂]
 b) Derive an expression for average and RMS value of sine wave. 8 CO1 [K₂]
