



B.E/B.TECH DEGREE EXAMINATIONS: NOV/DEC 2024

(Regulation 2018)

Fourth Semester

ELECTRICAL AND ELECTRONICS ENGINEERING

U18EET4004 Networks and Systems

COURSE OUTCOMES

- CO1:** Understand the basic concepts of graph theory and apply them to electrical networks.
CO2: Analyze the transient behavior of DC and AC circuits.
CO3: Model networks in the S-domain and determine their equivalent two-port network parameters.
CO4: Design various types of filters and attenuators and observe their frequency response.
CO5: Categorize the different types of signals and systems.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 2 = 20 Marks)

(Answer not more than 40 words)


- | | | |
|--|-----|-------------------|
| 1. Differentiate between a planar and non-planar graph. | CO1 | [K ₂] |
| 2. Define the terms "tree" and "co-tree" in network topology. | CO1 | [K ₁] |
| 3. What is the time constant in an RL circuit, and why is it significant? | CO2 | [K ₂] |
| 4. Describe how the capacitor's behavior changes between transient and steady states in an RC circuit. | CO2 | [K ₂] |
| 5. What is meant by the term "transform impedance"? | CO3 | [K ₁] |
| 6. Define poles and zeros in the network function. | CO3 | [K ₁] |
| 7. What is the role of cutoff frequency in a filter design? | CO4 | [K ₂] |
| 8. What are the classifications of filter? | CO4 | [K ₁] |
| 9. Discuss the key differences between a periodic and an aperiodic signal. | CO5 | [K ₂] |
| 10. List some examples for continuous signals. | CO5 | [K ₁] |

Answer any FIVE Questions:-


PART B (5 x 16 = 80 Marks)

(Answer not more than 400 words)


- | | | | |
|---|----|-----|-------------------|
| 11. a) What are the properties of a tree in network topology? | 04 | CO1 | [K ₂] |
| b) Write down the fundamental loop matrix of the network shown in below figure and find the loop current using tie set matrix method. | 12 | CO1 | [K ₃] |

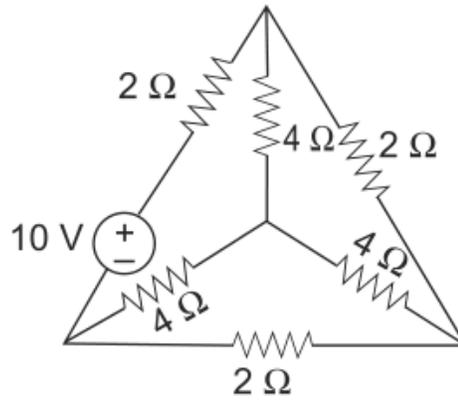

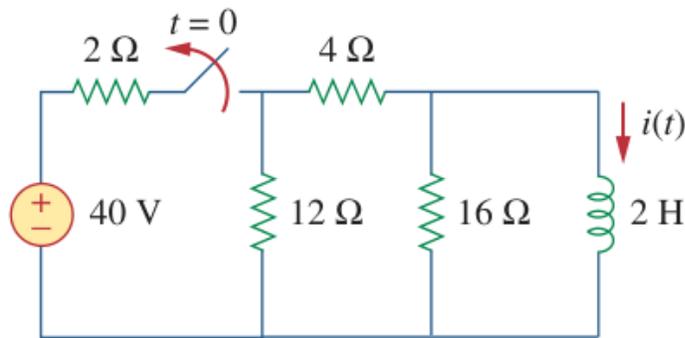12. a) The switch in the circuit of below figure has been closed for a long time. At $t=0$, the switch is opened. Calculate $i(t)$ for $t>0$. 08 CO2 [K₃]



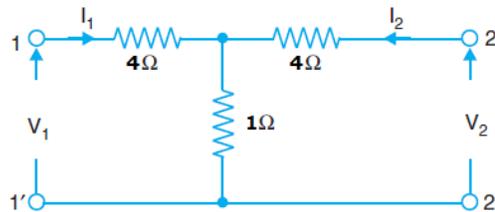- b) Derive the expressions for the transient current and voltage across the components of a series RC circuit when it is connected to a DC voltage source, assuming that the capacitor initially has no charge. 08 CO2 [K₂]
13. a) For the network shown in figure, find the Short Circuit Admittance Parameters. 06 CO3 [K₃]



- b) For the given network function, draw the pole zero diagram and obtain its time response. 10 CO3 [K₃]

$$I(S) = \frac{3S}{(S + 1)(S + 3)}$$

14. a) Design a T-pad attenuator to give an attenuation of 60 dB and to work in a line of 500 Ω impedance. Sketch the final circuit. 06 CO4 [K₃]

b) Derive the design parameters for a constant K high-pass filter and provide a diagram of the final circuit. 10 CO4 [K₂]

15. a) Check the stability of the system defined in the equation below. 10 CO5 [K₃]

$$h(n) = (1/4)^n U(n)$$

b) Check whether the given system is time invariant or time variant. 06 CO5 [K₃]

$$y(n) = x(2n)$$

16. a) Draw the graph corresponding to the given incidence matrix. 08 CO1 [K₃]

$$A = \begin{bmatrix} -1 & 0 & 0 & 0 & +1 & 0 & +1 & 0 \\ 0 & -1 & 0 & 0 & 0 & 0 & -1 & +1 \\ 0 & 0 & -1 & -1 & 0 & -1 & 0 & -1 \\ 0 & 0 & 0 & 0 & -1 & +1 & 0 & 0 \\ +1 & +1 & +1 & +1 & 0 & 0 & 0 & 0 \end{bmatrix}$$

b) Check the linearity of the system. 08 CO5 [K₃]

$$y(n) = x(n) + C$$
