





- a) To perform addition and subtraction operations      b) To rotate or shift data bits left or right in a single clock cycle
- c) To store data temporarily during computation      d) To convert analog signals to digital form
9. Assertion (A): Full custom design allows for maximum optimization of circuit performance and area. CO6 [K<sub>2</sub>]  
Reason (R): Semi-custom design methodologies provide a faster design cycle and lower initial costs compared to full custom design.
- a) Both A and R are true and R is the correct explanation of A      b) Both A and R are true but R is not the correct explanation of A
- c) A is true but R is false      d) A is false but R is true
10. Identify the statement that is true regarding FPGAs. CO6 [K<sub>2</sub>]
- a) FPGAs are programmable only once after manufacturing.      b) FPGAs consist of a fixed hardware architecture with no ability to configure logic functions.
- c) FPGAs can be reprogrammed multiple times to implement different functions or applications.      d) FPGAs are primarily used for applications that require high-speed processing with fixed logic.

**PART B (10 x 2 = 20 Marks)**  
**(Answer not more than 40 words)**

11. List the regions of operation for an N-MOSFET with its voltage levels. CO1 [K<sub>1</sub>]
12. Justify the reason for using PMOS as pull-up network. CO2 [K<sub>2</sub>]
13. Implement AND gate using pass transistor logic. CO3 [K<sub>2</sub>]
14. Recall Elmore's Constant. CO3 [K<sub>2</sub>]
15. Define propagation delay. CO5 [K<sub>1</sub>]
16. List the performance parameters of digital circuits. CO5 [K<sub>1</sub>]
17. List any two data path circuits. CO4 [K<sub>1</sub>]
18. State the purpose of ALU. CO4 [K<sub>1</sub>]
19. List any two importance of FPGA CO6 [K<sub>1</sub>]
20. Recall standard cell design. CO6 [K<sub>1</sub>]

**Answer any FIVE Questions:-**  
**PART C (5 x 14 = 70 Marks)**  
**(Answer not more than 350 words)**

- |     |    |  |   |     |                   |
|-----|----|--|---|-----|-------------------|
| 21. | a) | Construct the stick diagram of NAND gate realized using static CMOS logic.   | 7 | CO2 | [K <sub>3</sub> ] |
|     | b) | Summarize about the scaling principles of transistor.  | 7 | CO2 | [K <sub>2</sub> ] |
| 22. | a) | Construct the circuit of a 2:1 Multiplexer using pass transistor and transmission gate logic, and provide a detailed explanation of its working. | 7 | CO3 | [K <sub>3</sub> ] |
|     | b) | Describe in detail about the static and dynamic power dissipation  | 7 | CO3 | [K <sub>2</sub> ] |
| 23. | a) | Describe the characteristics and functionalities of static and dynamic latches in digital circuits.  | 7 | CO4 | [K <sub>2</sub> ] |
|     | b) | Discuss in detail the timing issues encountered in sequential circuits.  | 7 | CO4 | [K <sub>2</sub> ] |
| 24. | a) | Construct the architecture of 4 bit array multiplier in digital circuits.  | 7 | CO5 | [K <sub>3</sub> ] |
|     | b) | Discuss the speed and area trade-offs associated with different types of adders used in arithmetic operations.                                   | 7 | CO5 | [K <sub>3</sub> ] |
| 25. | a) | Compare full custom and semi-custom design methodologies in VLSI.  | 7 | CO6 | [K <sub>2</sub> ] |
|     | b) | Explain the routing procedures used in FPGAs, explaining the steps involved from logic block placement to programming the FPGA.                  | 7 | CO6 | [K <sub>2</sub> ] |
| 26. | a) | Discuss the operational principles and characteristics of PMOS and NMOS transistors in digital circuits.   | 7 | CO1 | [K <sub>2</sub> ] |
|     | b) | Elaborate on the functioning and significance of the CMOS inverter, including its advantages and applications in integrated circuits.            | 7 | CO1 | [K <sub>2</sub> ] |

\*\*\*\*\*