



**B.E/B.TECH DEGREE EXAMINATIONS: NOV/DEC 2024**

(Regulation 2024)

First Semester

**ELECTRONICS AND COMMUNICATION ENGINEERING**

24ECT101: Network Theory

**COURSE OUTCOMES**

- CO1:** Apply circuit laws and network theorems to solve complex DC circuits, including Delta-Star and Star-Delta transformations.
- CO2:** Analyze AC circuits using phasor representation and two-port network parameters to determine impedance, admittance, and related parameters.
- CO3:** Evaluate AC power analysis techniques to optimize power transfer and perform power factor correction in complex circuits.
- CO4:** Examine the transient and steady-state behaviour of first-order and second-order circuits to predict their response to various inputs.
- CO5:** Design resonance and coupled circuits by calculating mutual inductance and analyzing energy transfer characteristics in passive filters.


**Time: Three Hours**

**Maximum Marks: 100**

**PART A (4 \* 20 = 80 Marks)**

**Answer all the Questions**

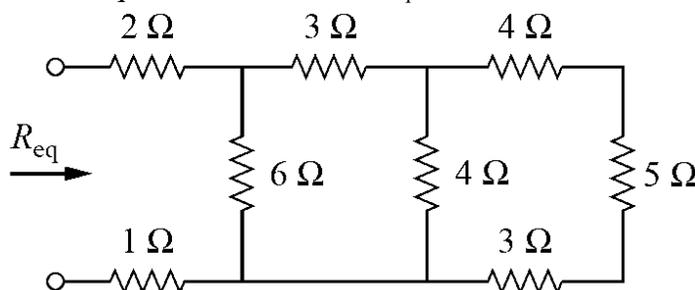
1. a) State and explain Kirchoff's Current Law (KCL). 2 CO1 [K<sub>2</sub>]
- b) Find the equivalent resistance  $R_{eq}$ . 2 CO1 [K<sub>2</sub>]



**Scenario:**


- c) A network with resistors  $R_a = 15\Omega$ ,  $R_b = 10\Omega$ , and  $R_c = 25\Omega$  in a Delta configuration is to be converted to Star. Calculate the equivalent resistances.

6 CO1 [K<sub>3</sub>]

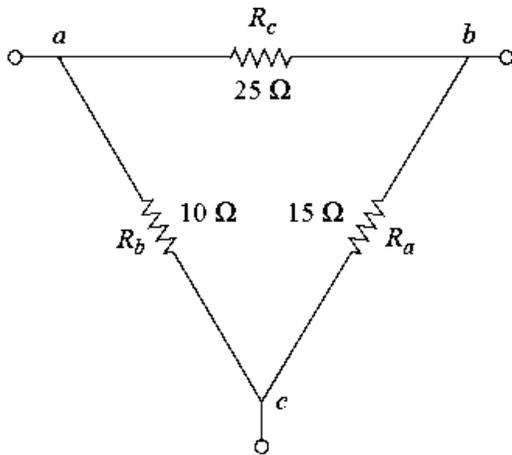


- d) Using Superposition Theorem, solve for  $V_0$  in the circuit with multiple sources: a 10V voltage source and a 4A current source.

6 CO1 [K<sub>3</sub>]

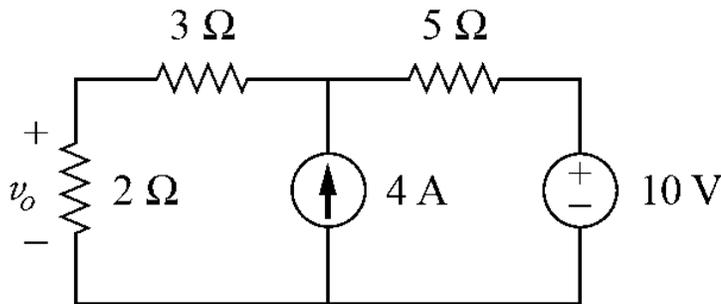

- e) Derive the expressions for  $V_L$  &  $I_L$  with the given Thevenin equivalent DC circuit.

4 CO1 [K<sub>4</sub>]

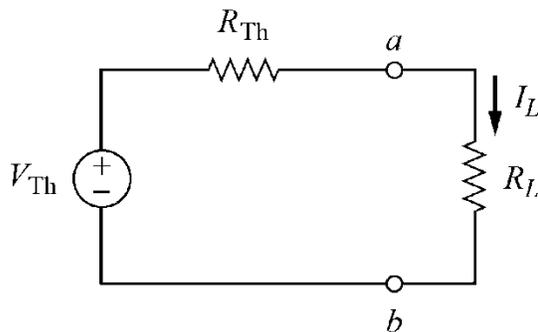


2. a) Define phasor representation and its importance in AC circuit analysis.  
 b) Compare impedance and admittance in AC circuits.

2 CO2 [K<sub>2</sub>]

2 CO2 [K<sub>2</sub>]

- c) Solve for the phasor currents in an AC series circuit with  $R = 10\Omega$ ,  $L = 0.2H$ , and supply voltage  $V = 220V$ ,  $f = 50Hz$ . 6 CO2 [K<sub>3</sub>]
- d) Determine the Z-parameters for a two-port network with input voltages and currents  $V_1 = 12V$ ,  $V_2 = 6V$ ,  $I_1 = 1A$ ,  $I_2 = 0.5A$ . 6 CO2 [K<sub>3</sub>]
- e) Differentiate between Transmission (ABCD) and Hybrid (H) parameters in a two-port network. 4 CO2 [K<sub>4</sub>]

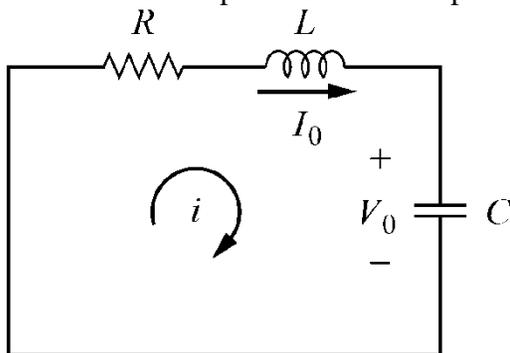3. a) Define the step response of an RL circuit. 2 CO4 [K<sub>2</sub>]
- b) Explain the transient behavior of a source-free RC circuit. 2 CO4 [K<sub>2</sub>]
- c) Analyze the given series RLC circuit with  $R = 40\Omega$ ,  $L = 4H$  &  $C = 0.2 F$  and find whether the response is over damped or critically damped or under damped. 6 CO4 [K<sub>4</sub>]



- d) A series RC circuit with  $R = 1k\Omega$  and  $C = 10\mu F$  is connected to a 10V step input. Calculate the voltage across the capacitor after 1ms. 6 CO4 [K<sub>3</sub>]
- e) Discuss the significance of the time constant in first-order circuits. 4 CO4 [K<sub>2</sub>]
4. a) Define resonance in series RLC circuits. 2 CO5 [K<sub>1</sub>]
- b) Derive the expression for the coefficient of coupling in magnetically coupled circuits. 2 CO5 [K<sub>2</sub>]
- c) **Problem:** A series RLC circuit with  $R = 20\Omega$ ,  $L = 0.1H$ ,  $C = 10\mu F$  is connected to a 230V, 50Hz source. Determine:  
 i) Resonant frequency,  
 ii) Half power frequencies,  
 iii) Impedance at resonance,  
 iv) Bandwidth,  
 v) Quality factor. 12 CO5 [K<sub>4</sub>]
- d) Design a low-pass filter using passive components. Provide the circuit diagram and explain its working. 4 CO5 [K<sub>3</sub>]

**PART B (1x 20 = 20 Marks)**  
**Answer any ONE Question**

5. a) Define RMS value. 2 CO3 [K<sub>2</sub>]
- b) Differentiate between active power and apparent power. 2 CO3 [K<sub>2</sub>]
- c) For a circuit with  $R = 20\Omega$ ,  $L = 0.15H$ , and  $C = 100\mu F$ , connected to a 230V, 50Hz supply, calculate: 6 CO3 [K<sub>3</sub>]  
 i) Current,  
 ii) Power factor,  
 iii) Power consumed.
- d) Discuss the importance of power factor correction in industrial power systems. 6 CO3 [K<sub>4</sub>]
- e) Explain the role of complex power in AC circuit analysis. 4 CO3 [K<sub>2</sub>]

OR

6. a) Define average power. 2 CO3 [K<sub>2</sub>]
- b) What is power factor? State its application in AC circuits. 2 CO3 [K<sub>2</sub>]
- c) Derive the Z-parameters for a two-port network. 12 CO2 [K<sub>3</sub>]
- d) Compare series and parallel resonance circuits in terms of bandwidth and Q-factor. 4 CO5 [K<sub>4</sub>]

CO distribution summary:

	CO1	CO2	CO3	CO4	CO5
Marks (%)	20	20	20	20	20

\*\*\*\*\*