



B.E/B.TECH DEGREE EXAMINATIONS: NOV/DEC 2022

(Regulation 2018)

Third Semester

ELECTRONICS & INSTRUMENTATION ENGINEERING

U18EII3202 : Sensors and Measurements

COURSE OUTCOMES

CO1: CO1: Describe the characteristics and construction details of different sensors.

CO2: CO2: Analyze suitable signal conditioning circuits for resistive, reactance, and self-generating sensors.

CO3: CO3: Explain the fundamental concepts and working principle of analog and digital meters.

CO4: CO4: Analyze the specification details for the given sensor/Instrument.

Time: Three Hours

Maximum Marks: 100

Answer all the Questions:-

PART A (10 x 1 = 10 Marks)

1. Match the following:

CO1 [K₂]

List I	List II
A. LVDT	i. Displacement sensitive
B. Capacitive Type Transducer	ii. Motion Transducer
C. Piezo-electric Transducer	iii. Magnetic Coupling
D. Electromechanical Type Transducer	iv. Crystalline Material

- | | A | B | C | D |
|----|-----|----|----|-----|
| a) | iii | ii | i | iv |
| b) | i | iv | ii | iii |
| c) | iii | iv | i | ii |
| d) | iii | i | iv | ii |

2. Dead zone of an instrument is


CO1 [K₁]

- | | |
|--|--|
| a) The largest change of input quantity for which there is no output of the instrument | b) The time required by an instrument to begin to respond to a change in measurand |
| c) The unmeasured quantity which exceeds the maximum range of the instrument | d) The time required by an instrument to warm up initially |


3. Which of the following are piezoelectric substances?

CO4 [K₁]

- | | |
|-------------------------|---------------|
| 1. Barium titanate | |
| 2. Lead titanate | |
| 3. Lead Zirconate | |
| 4. Cadmium and sulphate | |
| a) 1, 2 and 4 | b) 1, 3 and 4 |

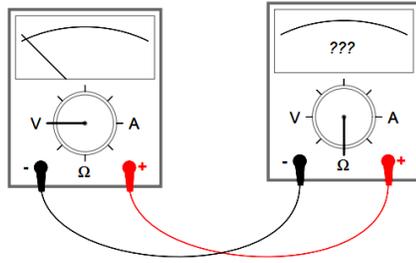

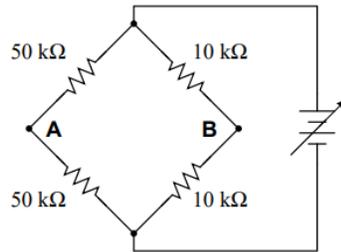
13. State the dynamic characteristics of a simplified measuring system. CO1 [K₁]
 14. What will happen to the voltage between points A and B if the power supply voltage increases? CO3 [K₃]
 Justify.




15. List out the types of input circuits used in signal conditioning. CO2 [K₂]
 16. Define inverse transducer with an example. CO1 [K₁]
 17. Suggest sensors that could be used in the following situations: CO4 [K₃]
 a) To monitor the displacement of a rod and give a voltage output.
 b) To monitor a rapidly changing temperature.
 18. Write any four basic requirements of the transducer. CO4 [K₂]
 19. What is a resolver to digital converter? CO2 [K₁]
 20. Name the Biosensor used for pregnancy test. CO2 [K₂]

**Answer any FIVE Questions:-
 PART C (5 x 14 = 70 Marks)
 (Answer not more than 350 words)**

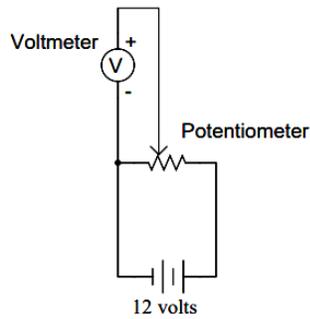21. a) Describe the functional elements of an instrument with its block diagram. 10 CO1 [K₂]
 b) Distinguish between 4 CO1 [K₂]
 i) Accuracy and Precision
 ii) Range and Span
 22. a) Which electromagnetic sensor is used to sense the angular position of a shaft? 12 CO4 [K₃]
 Explain the same in detail with necessary schematic diagram.
 b) What would you expect the voltmeter in the following circuit to do when the potentiometer wiper is moved to the right? 2 CO4 [K₃]



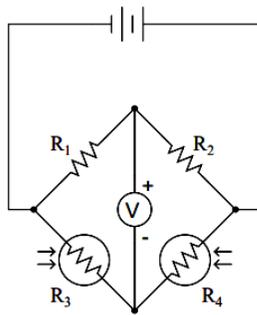23. a) Describe the construction and function of a moving iron voltmeter with the required diagrams. 10 CO3 [K₂]
- b) This bridge circuit is supposed to generate an output voltage proportional to the difference between light exposure on the two photocells: 4 CO3 [K₄]



However, something has failed in this circuit, because the voltmeter is "pegged" fully negative and was not changing with varying light exposures on the two cells. Identify at least two possible failures that could cause the voltmeter to over-range in the negative direction.

24. With a neat sketch explain the operation of LVDT. List its advantages and disadvantages. 14 CO2 [K₂]
25. a) With the aid of neat sketch, explain the working principle of piezoelectric transducer. Also, discuss its different modes of operation. 10 CO4 [K₂]
- b) State the properties of piezoelectric crystals. 4 CO4 [K₂]
26. a) What are intelligent sensors? State their components and discuss their features. 10 CO1 [K₂]
- b) Recall the different types of thermocouple and the materials used for constructing each type. 4 CO1 [K₂]
